

# The 1Volt QRP Transceiver

## The 1 Volt Antenna

Design: Helmut Seifert DL2AVH  
PCB Layout: Gero Schusser DL4ALJ



### Our Goals:

Save the resources of our earth, save the earth  
Reduce battery waste  
Reduce required materials  
As much fun as possible, so make a **real** useful **transceiver**


Modern solid state technologie makes it possible to design RF transmitters and receivers with a powers supply as low as 1 Volt with good efficiency. The mainly power consuming parts, the AF end-amplifier and the RF-PA have to be designed very carefully to give good results and to meet the goals. The efficiency today would be optimal at 3 Volt. This experimental design will be the base for a 3 Volt Transceiver with an RF power of > 0.5 Watt.

<b>Results:</b>	$U_{\text{Batterie}}$	$I_{\text{RX}}$	$U_{\text{AF-max}}$	$I_{\text{Tx}}$	$P_{\text{out at 50 Ohm}}$
	1.1 Volt	5 mA	0.73V <sub>pp</sub>	0.2A	80mW
	1.3 Volt	7 mA	0.89V <sub>pp</sub>	0.27A	130mW
	1.5 Volt	9 mA	0.97V <sub>pp</sub>	0,33A	180mW

Gain :  $U_{\text{AF-out}} / U_{\text{RF-in}} = 90 \text{ dB}$   
2<sup>nd</sup> harmonic -32 dB, 3<sup>rd</sup> harmonic -42 dB

What´s a txvr withot an antenna? Nothing! So we designed **The 1 Volt Antenna** matching the new transceiver. It is an ultralight high efficiency portable antenne which (if packed) is as small as the transceiver. It needs no ATU and no transmission line.

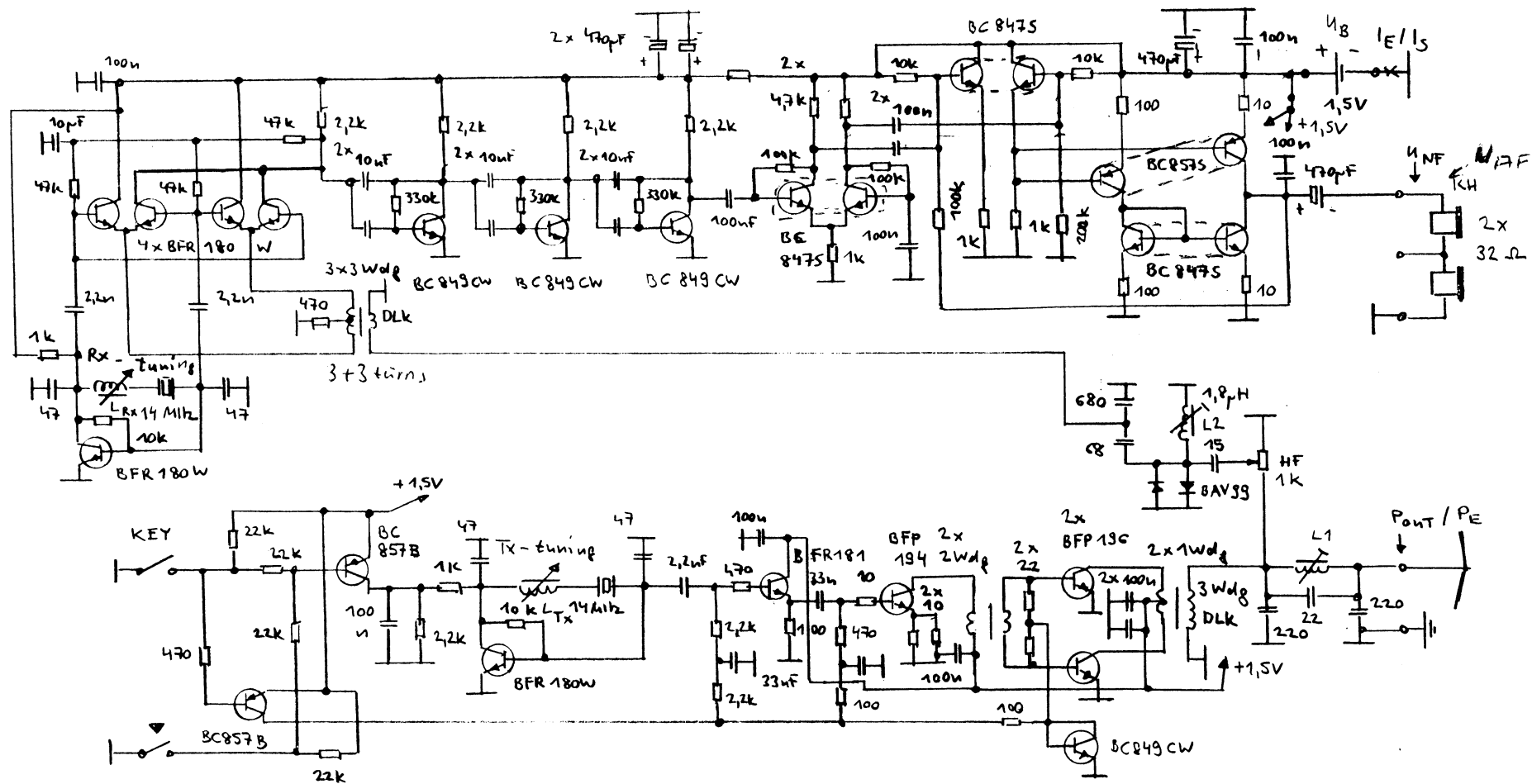DL-QRP-AG Activity group QRP and homebrew, the German language QRP Club  
Homepage: <http://www.dl-qrp-ag.de>  
Contact: DL2FI@dl-qrp-ag.de



L1 8 turns 0,2mm enamel wire on Neosid 7.1k / 9,5nH  
 L2 1,8 uH Neosid 7A-04, Q=110 / 10 MHz  
 LRX=LTX 30 turns 0,14 mmenamel wire on Neosid 7.1k / 9,5nH  
 DLK=DoubleHole (pig-nose) 4,6\*7,6\*4mm 0,8 uH /WL

U <sub>batterie</sub>	I <sub>RX</sub>	U <sub>AF-max</sub>	I <sub>TX</sub>	O <sub>-out at 50 Ohm</sub>
1.1V	5mA	0.73Vpp	0.2A	80mW
1.3V	7mA	0.89Vpp	0.27A	130mW
1.5V	9mA	0.97Vpp	0.33A	180mW




RX -3dB=600/1100 Hz -10dB=1600Hz -20dB=2000Hz

Gain RX  $U_{AF}/U_{RF}=90\text{dB}$

Pig nose  $0.8 \mu\text{H/WL}$   
4 turns

300cm

645cm

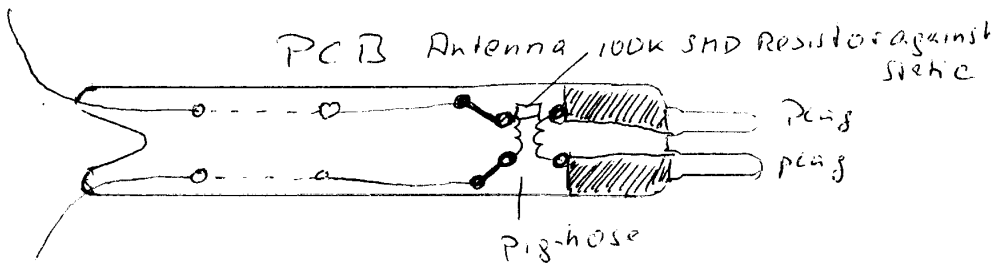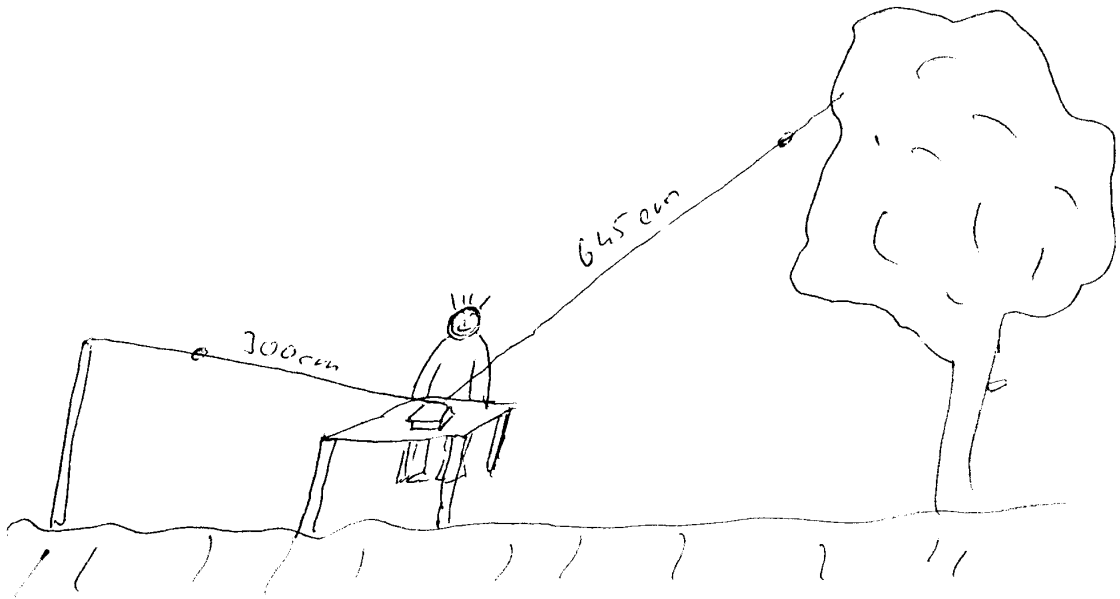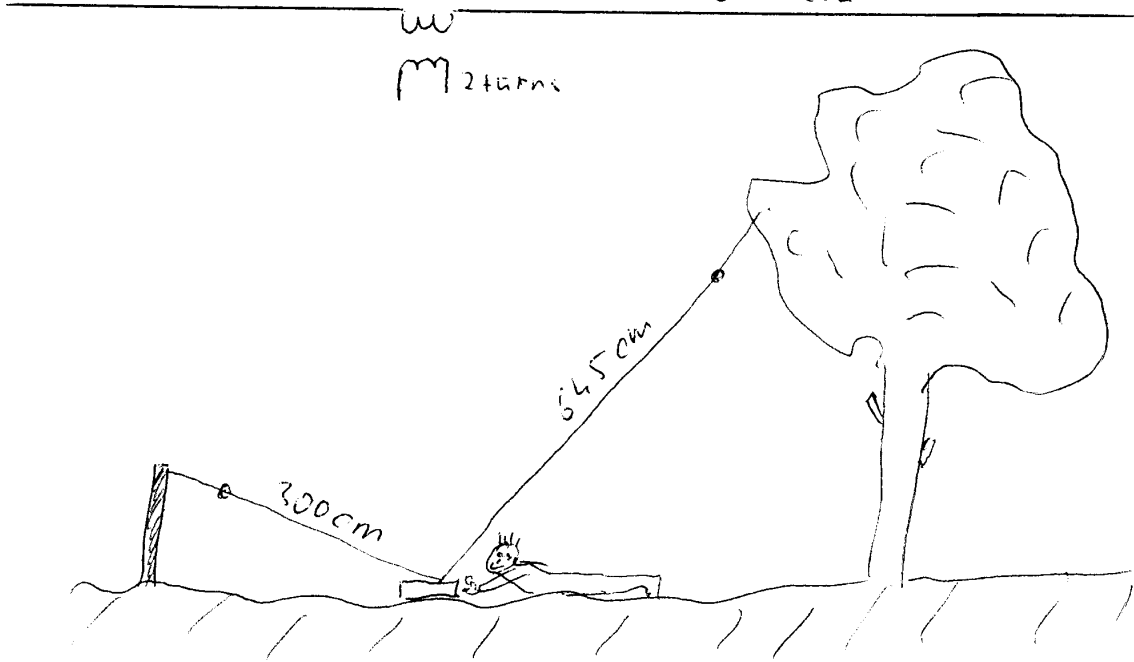



1Volt transceiver top view



1 Volt Antenna